

DC-DC Converter

B Swaroop Reddy and G V V Sharma*

CONTENTS

1	Components	1
2	Circuit Operation	1
3	Circuit Assembly	2
4	Fourier Series Analysis of Buck-Converter	3

Abstract—This manual provides the design of a DC-DC Buck-Converter.

1 COMPONENTS

Component	Value	Quantity
Arduino Uno		1
Inductor	5 mH	1
Capacitor	10 uF	1
n-MOS	IRF 540	1
Jumper Wires	M-M	20
Diode		1
Gate Driver	TLP350	1

TABLE I

2 CIRCUIT OPERATION

The buck converter blockdiagram and circuit is shown in Fig. 1 and Fig. 2.

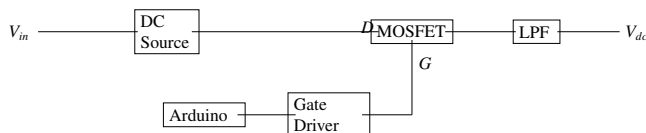


Fig. 1: Block Diagram

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

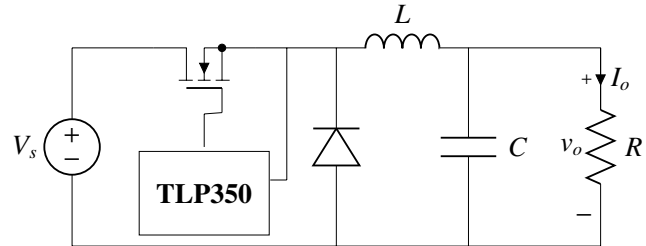


Fig. 2: DC-DC buck converter

Problem 2.1. When the switch is ON, the circuit diagram is shown in Fig. 3. Express the voltage across inductor in terms of V_s and V_o and current passing through the capacitor in terms of I_L and I_o when switch is ON.

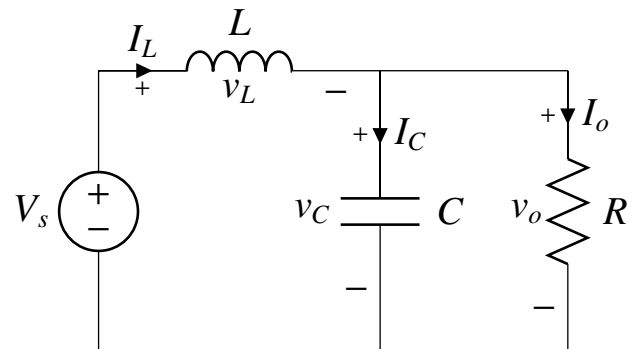


Fig. 3: Switch in ON state

Solution:

$$V_L(ON) = V_s - V_o$$

$$I_C(ON) = I_L - I_o$$

Problem 2.2. When the switch is OFF, the circuit diagram is shown in Fig. 4. Express the voltage across inductor in terms of V_s and V_o and current passing through the capacitor in terms of I_L and I_o when switch is OFF.

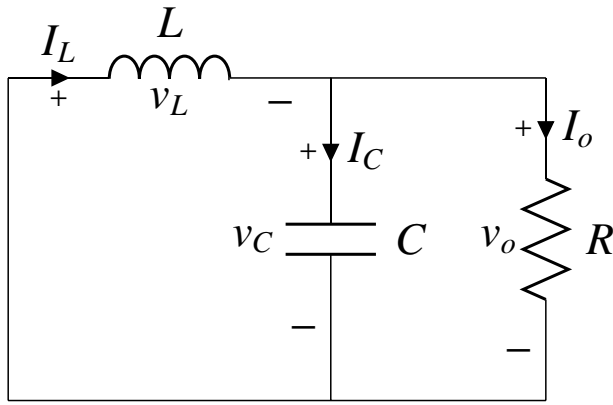


Fig. 4: Switch in OFF state

Solution:

$$V_L(OFF) + V_o = 0$$

$$V_L(OFF) = -V_o$$

$$I_C(OFF) = I_L - I_o$$

Problem 2.3. Find V_o and I_o .**Solution:** From Volt-sec Balance

$$V_L(ON)T_{ON} + V_L(OFF)T_{OFF} = 0$$

$$(V_s - V_o)DT - V_o(1 - D)T = 0$$

$$V_o = DV_s$$

Where D is Duty cycle. From Amp-sec Balance,

$$(I_L - I_o)DT + (I_L - I_o)(1 - D)T = 0$$

$$I_o = I_L$$

Problem 2.4. Express L in terms of D, V_o , $f = \frac{1}{T}$ and ΔI_L where ΔI_L is Ripple in the inductor current i.e maximum change in the inductor current from ON state to OFF state .

Solution:

$$V_L(ON) = V_s - V_o$$

$$L \frac{di_{ON}}{dt_{ON}} = V_s - V_o$$

$$L \frac{\Delta I_L}{DT} = V_s - DV_s$$

$$L = \frac{D(1 - D)V_s}{\Delta I_L f}$$

$$L = \frac{(1 - D)V_o}{f \Delta I_L} \quad (2.4.1)$$

Where ΔI_L is Ripple in the inductor current i.e

maximum change in the inductor current from ON state to OFF state .

Problem 2.5. Express C in terms of L, D, ΔV_o and $f = \frac{1}{T}$.

Solution: Charge on the capacitor

$$Q = CV_C$$

$$\Delta Q = C \Delta V_C = C \Delta V_o$$

 ΔQ =Area under the capacitor current will

$$\Delta Q = \frac{1}{2} \frac{\Delta I_L}{2} \frac{T}{2} = \frac{\Delta I_L}{8f}$$

$$C = \frac{\Delta I_L}{8f \Delta V_o} \quad (2.5.1)$$

Problem 2.6. Assume,Input Voltage (V_s) = 10VOutput Voltage (V_o) = 5V ΔI_L = 11% of I_L ΔV_o = 6% of V_o Let $R = 5\Omega$ (for $I_o = 1A$)

Calculate L and C.

Problem 2.7. Connect the circuit as per the Fig. 2 and measure I_o and V_o .

3 CIRCUIT ASSEMBLY

Problem 3.1. Assemble the Buck converter circuit according to Figs. 1, 5 and Table II.

TLP350	1	2	3	4	5	6	7	8
ARDUINO	NA	13	GND	NA			NA	
					GND			15V
						22 Ω		

TABLE II: Pin Connections

Problem 3.2. Program the arduino to generate a square wave with *Duty Cycle* $D = 0.5$ and frequency $f = 5KHz$.

Solution:


```

void setup() {
    pinMode(13, OUTPUT);
}

void loop() {
    digitalWrite(13, LOW);

```

Pin Configuration

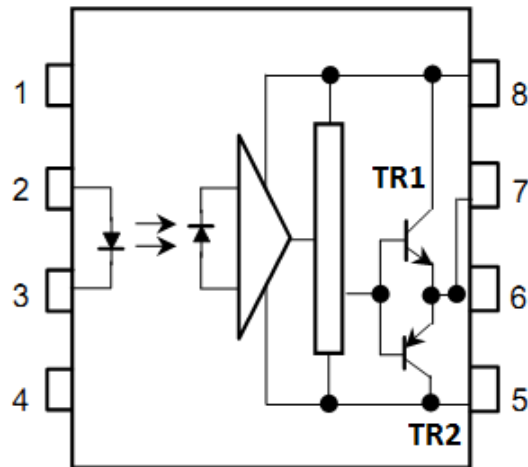

- 1 : N.C.
- 2 : Anode
- 3 : Cathode
- 4 : N.C.
- 5 : GND
- 6 : V_O (Output)
- 7 : V_O
- 8 : V_{CC}

Fig. 5: TLP350

```
delayMicroseconds(10);
digitalWrite(13,HIGH);
delayMicroseconds(10);
}
```

4 FOURIER SERIES ANALYSIS OF BUCK-CONVERTER

Problem 4.1. Observe the output of the Source pin of the n-MOS on oscilloscope and write the python script to generate the same.

Solution: The output is shown in Fig. 6

```
import numpy as np
import matplotlib.pyplot as plt
from scipy import signal
A = 10 # wave amplitude

T = 0.2 # wave period
```

```
t = np.linspace(-2.5*T, 2.5*T, int(1e4))

plt.plot(t, A/2 * (1 + signal.square(2*np.pi*t/T, 0.5)))

plt.ylim(-1, 12)
plt.grid()
plt.xlabel('$t(msec)$')
plt.ylabel('$X(t)$')
plt.savefig('square.eps')
plt.show()
```

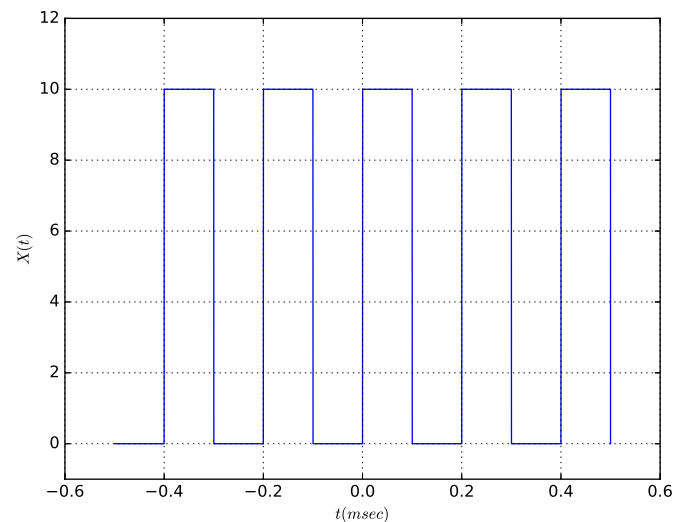


Fig. 6: Square Pulse

Problem 4.2. Show that the voltage across the diode in Fig. 1 is

$$V_D(t) = \begin{cases} \sum_{n=1}^{\infty} \frac{10}{n\pi} \sin(2\pi f t) & n \text{ odd} \\ 5 & n = 0 \\ 0 & n \text{ even} \end{cases} \quad (4.2.1)$$

Problem 4.3. Compute and sketch the frequency response for the L-C-R part of Fig. 1 shown in Fig. 7 for $R = 5\Omega$ and L and C calculated using equation (2.4.1) and equation (2.5.1). What kind of filter is it?

Problem 4.4. Calculate the cut-off frequency for the filter in Fig. 6.

Problem 4.5. Find V_o .

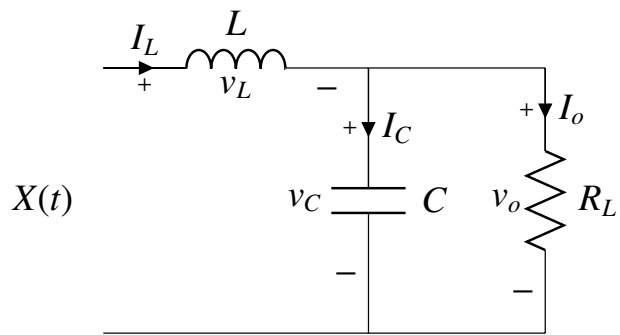


Fig. 7: Filter