

DC-AC Converter

B Swaroop Reddy and G V V Sharma*

CONTENTS

1	Components	1
2	Circuit Operation	1
3	Fourier Series Analysis of DC-AC Converter	2

Abstract—This manual provides the design of a DC-AC Converter.

1 COMPONENTS

Component	Value	Quantity
Arduino Uno		1
Capacitor	470 μ F, 25 V	4
Capacitor	220 μ F, 25 V	4
Capacitor	47 pF, 25 V	4
n-MOS	IRF 640	2
Diodes		6
Gate Driver	TLP350	2

TABLE I

2 CIRCUIT OPERATION

The DC-AC converter Block diagram and circuit are shown in Fig. 1 and Fig. 2

Problem 2.1. Generate two dc sources of +12 V and -5 V each using the voltage regulator circuit as shown in the Fig.3

Problem 2.2. Program the arduino to generate a square wave with *Duty Cycle* $D = 0.5$ and frequency

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

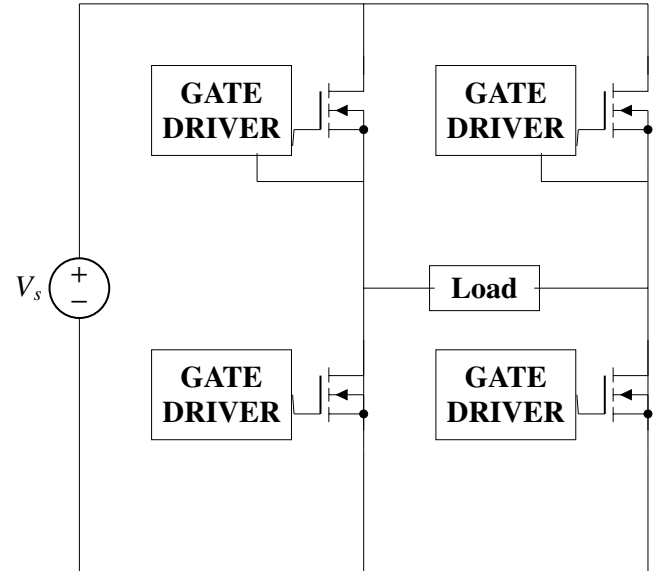


Fig. 1: DC-AC converter

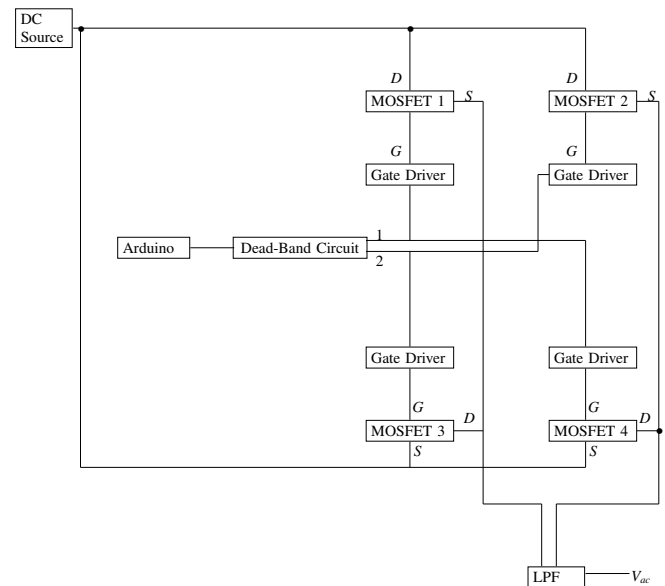


Fig. 2: DC-AC converter Block-diagram

$f = 50\text{Hz}$ and observe the waveform on the oscilloscope.

Solution:

```
void setup() {
  pinMode(13, OUTPUT);
}
```


Problem 3.4. Find the output of the lowpass filter designed in 3.3 with input as obtained from the result of 3.1. What do you observe?